

Sub: _____

Day

--	--	--	--	--	--	--	--

Time: _____

Date: / /

Name : Tanjim Reza

Student ID : 20101065

Course : CSE250

Section : CSE06

Lab Assignment : 03

Sub: _____

Day

Time: _____

Date: / /

Name of the Experiment: Verification of
KCL and KVL


KVL

Objective: This experiment is intended to verify Kirchhoff's voltage law (KVL) with the help of series circuits.

Theory: KVL states that around any closed circuit the algebraic sum of the voltage rises equals the algebraic sum of the voltage drops.

Apparatus: DC voltage source, Resistors, Ammeter and voltmeter.

Circuit/System Diagram:

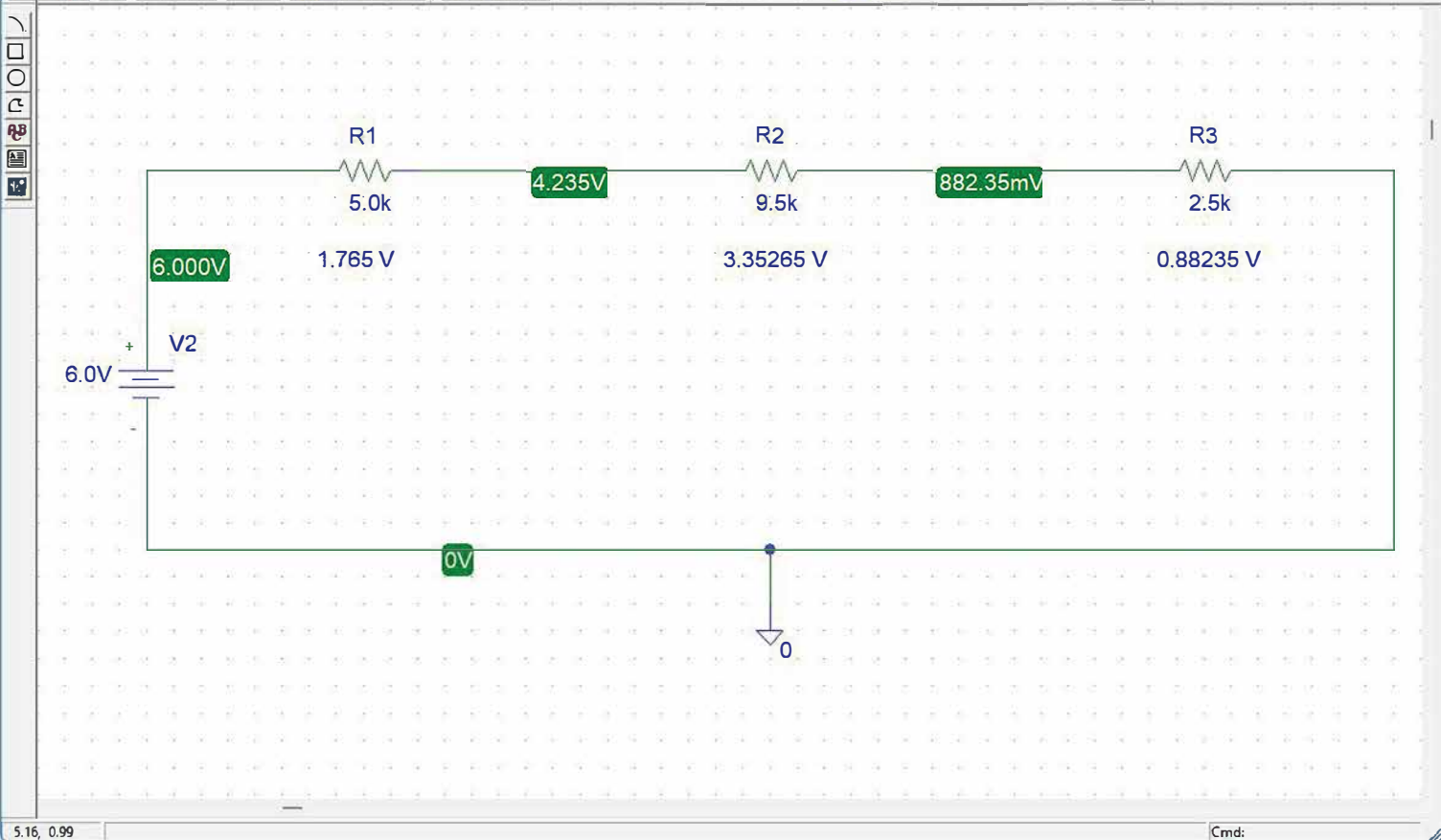

Result/Analysis:

Given,

$$R_1 = 5 \text{ k}\Omega$$

$$R_2 = 9.5 \text{ k}\Omega$$

$$R_3 = 2.5 \text{ k}\Omega$$

$$V_A = 6.0 \text{ V}$$

R_1, R_2, R_3 are connected in series.

$$R_{123} = (5 + 9.5 + 2.5) = 17 \text{ k}\Omega$$

Now, as all the resistors are in series, the current throughout the circuit will be constant

$$\begin{aligned} \therefore I &= \frac{V}{R} = \frac{V_A}{R_{123}} \\ &= \frac{6 \text{ V}}{17 \text{ k}\Omega} \\ &= \frac{6}{17} \text{ mA} \end{aligned}$$

Sub: _____

Day

Time

Date

According to the circuit, voltage across R_1, R_2, R_3 are V_1, V_2, V_3 .

$$\begin{aligned}\therefore V_1 &= I R_1 = \frac{6}{17} \times 5 \\ &= 1.7647 \text{ V} \\ &= 1.765 \text{ V}\end{aligned}$$

$$V_2 = I R_2 = \frac{6}{17} \times 9.5 = 3.352 \text{ V}$$

$$V_3 = I R_3 = \frac{6}{17} \times 2.5 = 0.882 \text{ V}$$

KVL verification Table:

Observation	R_1 ($\text{k}\Omega$)	R_2 ($\text{k}\Omega$)	R_3 ($\text{k}\Omega$)	V_A (V)	V_1 (V)	V_2 (V)	V_3 (V)	$V_1 + V_2 + V_3$ (V)
Simulation	5	9.5	2.5	6	1.765	3.352	0.882	6
Theoretical	5	9.5	2.5	6	1.765	3.352	0.882	5.999

Questions and Answers:

All box input questions are answered in the Result part showing the calculations. I have considered 5.999V as 6V.

And $V_1 + V_2 + V_3 = V$ this has been calculated and proved. (combined discussion in the end)

Sub: _____

Day

--	--	--	--	--	--	--	--

Time: _____

Date: / /

KCL


Objective: This experiment is intended to verify Kirchhoff's law (KCL) with the help of simple parallel circuit.

Theory:

KCL states that the algebraic sum of the currents entering any node equals the sum of the currents leaving the node.

Apparatus: DC Ammeter, Resistors, DC Power supply.

Circuit / System Diagram:

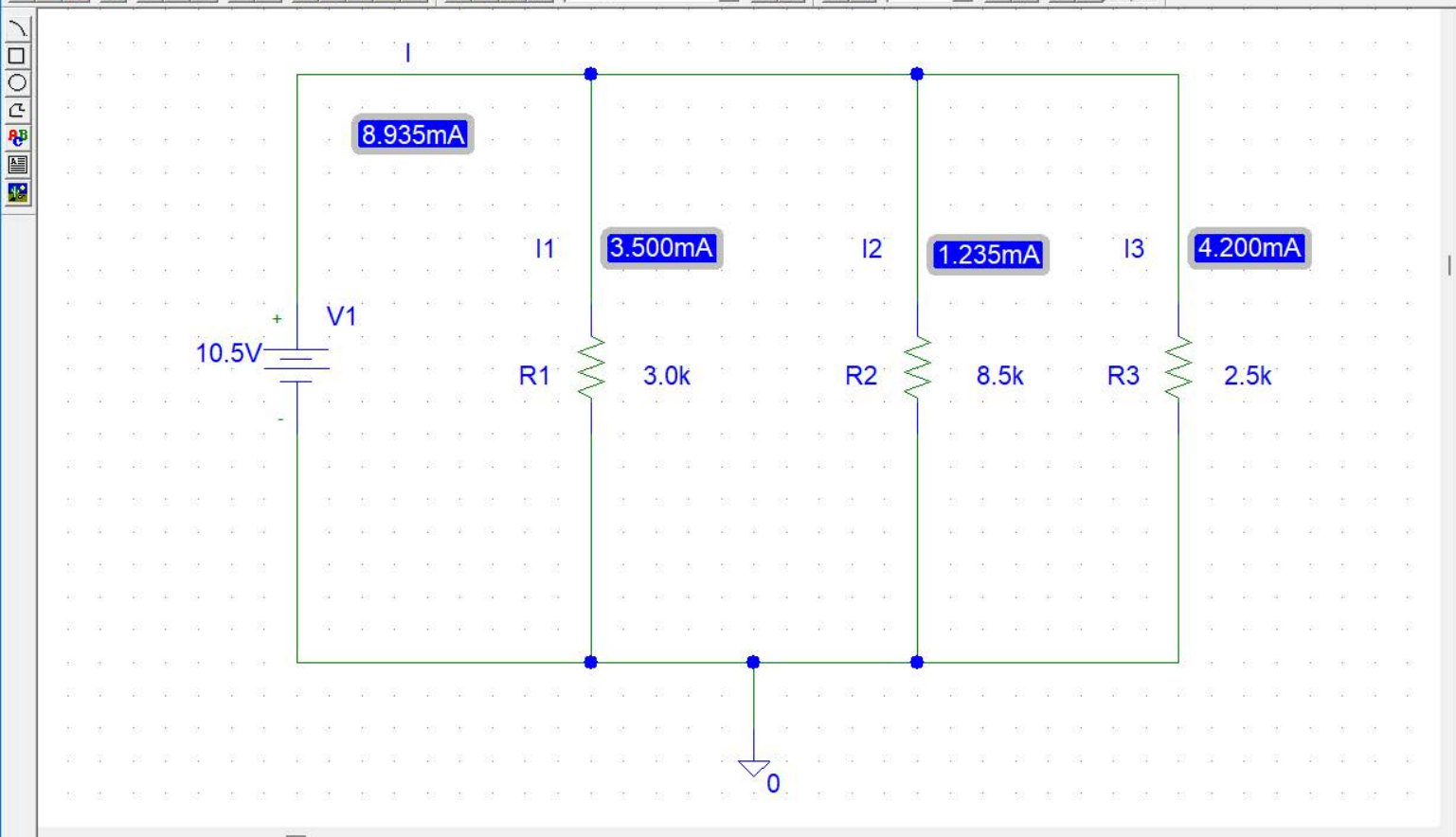

Result/Analysis:

Given,

$$R_1 = 3 \text{ k}\Omega$$

$$R_2 = 8.5 \text{ k}\Omega$$

$$R_3 = 2.5 \text{ k}\Omega$$

$$V_A = 10.5 \text{ V}$$

R_1 , R_2 and R_3 are in parallel connection

$$\therefore R_{123} = \left(\frac{1}{3} + \frac{1}{8.5} + \frac{1}{2.5} \right)^{-1}$$

$$= 1.175115207$$

$$= 1.1751 \text{ k}\Omega$$

We know,

$$V = IR$$

$$\Rightarrow I = \frac{V}{R} = \frac{10.5}{1.1751}$$

$$= 8.935 \text{ mA}$$

Sub: _____

Day

Time: _____

Date: / /

$$\therefore I_1 = \frac{V_1}{R_1} = \frac{V}{3} = \frac{10.5}{3} = 3.5 \text{ mA}$$

$$I_2 = \frac{V}{R_2} = \frac{10.5}{8.5} = 1.2352 \text{ mA}$$

$$I_3 = \frac{V}{R_3} = \frac{10.5}{2.5} = 4.2 \text{ mA}$$

$$\begin{aligned} I_1 + I_2 + I_3 &= (3.5 + 1.2352 + 4.2) \\ &= 8.935 \text{ mA} \\ &= I \end{aligned}$$

KCL verification Table:

Observation	R_1 (k Ω)	R_2 (k Ω)	R_3 (k Ω)	I (mA)	I_1 (mA)	I_2 (mA)	I_3 (mA)	$I_1 + I_2 + I_3$ (mA)
Simulation	3	8.5	2.5	8.935	3.500	1.235	4.200	8.935
Theoretical	3	8.5	2.5	8.935	3.5	1.235	4.2	8.935

Questions and Answers:

Value of I , I_1 , I_2 , I_3 have been calculated theoretically and also in simulation.

$(I_1 + I_2 + I_3)$ for both cases exactly matches with I which is what we wanted.

Finally, for both KVL and KCL our experiment has successfully succeeded.

For KVL,

$$V_1 + V_2 + V_3 = V$$

For KCL,

$$I_1 + I_2 + I_3 = I.$$

Sub: _____

Day

--	--	--	--	--	--	--

Time: _____

Date: / /

Discussions

The experiment proved the Law of KCL and KVL and the theoretical and simulated value were totally correct thereby verifies KVL and KCL