

Name : Tanjim Reza


Student ID : 20101065

Course : CSE 250

Section : CSE06

Assignment : 02

### Problem 01:

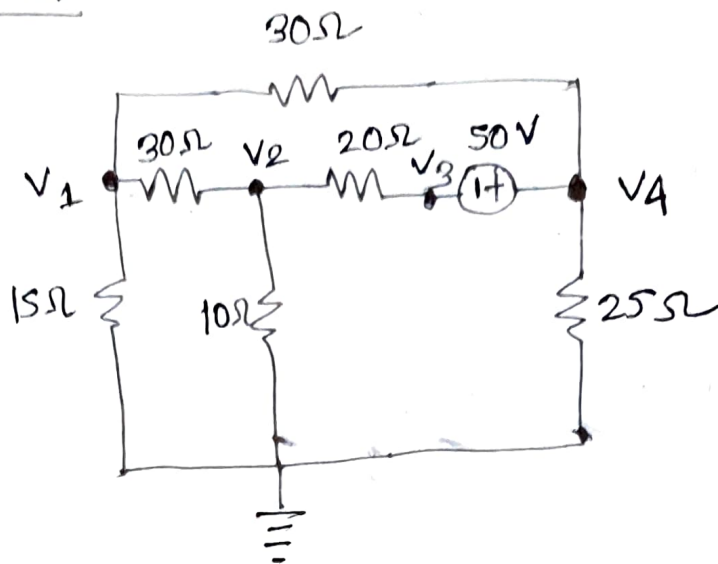

Node Equation for Node 01:

$$V_1 \left( \frac{1}{15} + \frac{1}{30} + \frac{1}{30} \right) - \frac{V_2}{30} - \frac{V_4}{30} = 0 \quad \left[ \frac{V_0}{15} = 0 \right]$$

Node 02:

$$V_2 \left( \frac{1}{30} + \frac{1}{10} + \frac{1}{20} \right) - \frac{V_1}{30} - \frac{V_3}{30} = 0$$

50V source:

(Positive - Negative)

$$\therefore V_4 - V_3 = 50$$

Node 3, 4 (supernode)

$$V_4 \left( \frac{1}{25} + \frac{1}{30} \right) - \frac{V_1}{30} + \frac{V_3}{20} - \frac{V_2}{20} = 0$$

Power for voltage source (50V)

$$P = VI$$

$$= (V_4 - V_3) \left( \frac{V_3 - V_2}{20} \right) \quad (\text{Already considered for sign})$$

Solving Node Equations with calculator

$$V_1 = 2.24252 \text{ V}$$

$$V_2 = -8.47176 \text{ V}$$

$$V_3 = -32.5581 \text{ V}$$



$$V_4 = 17.4419 \text{ V}$$

$$\therefore P = -60.21585 \text{ Watt}$$


(took all values from calculator)

Negative means supplying.


Problem 02:

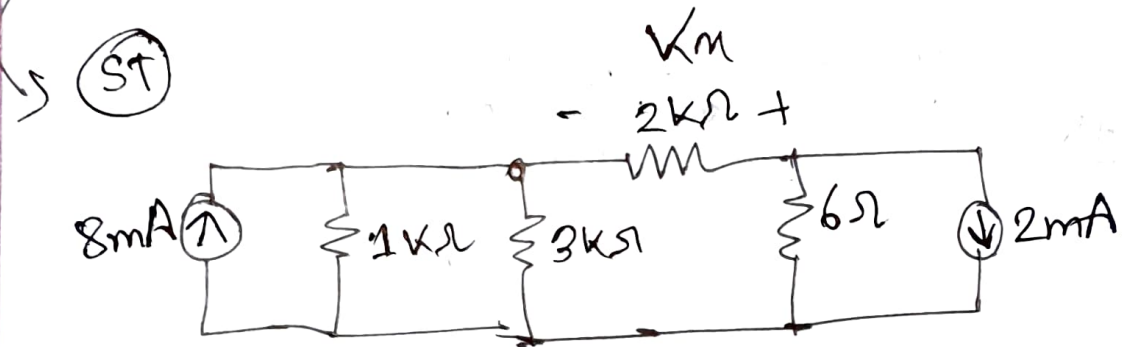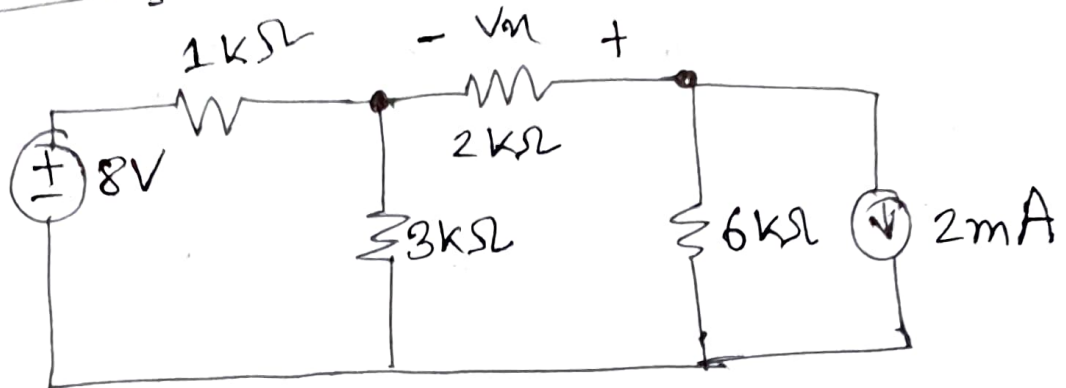


Taking  $1k\Omega$  &  $3k\Omega$

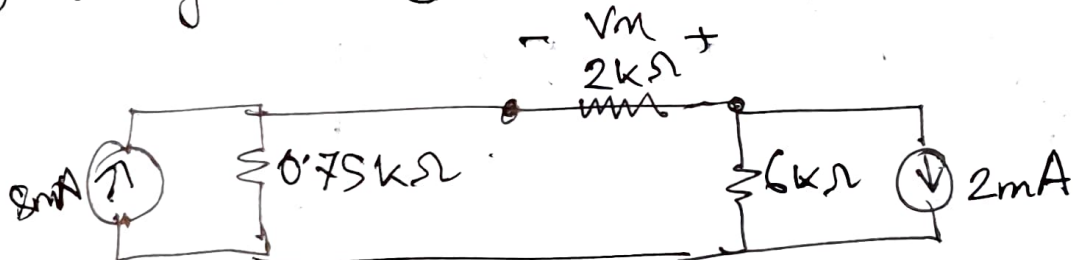


ST  $6k\Omega$  &  $2mA$

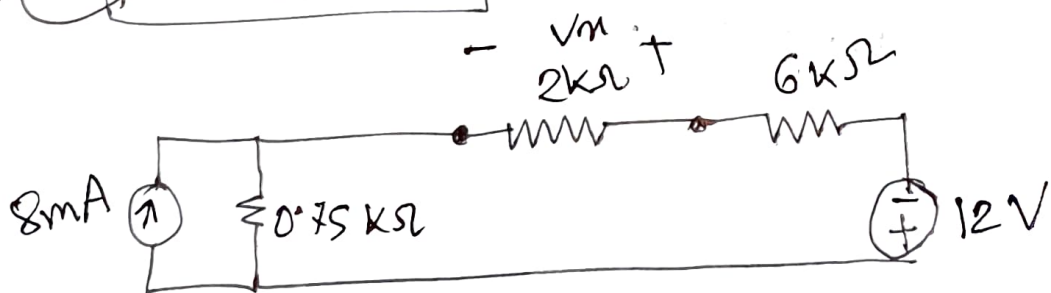

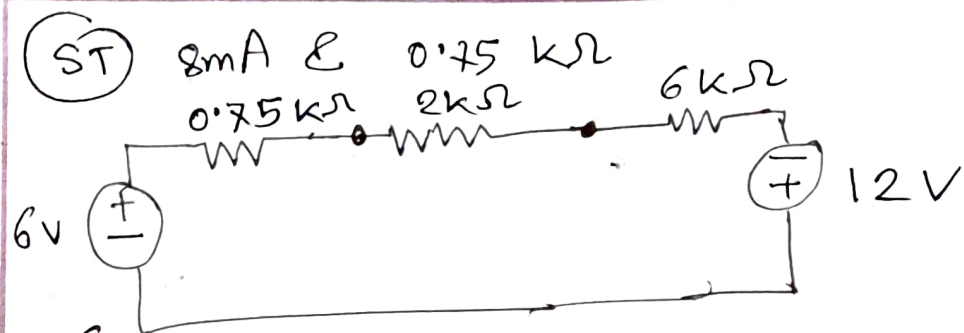

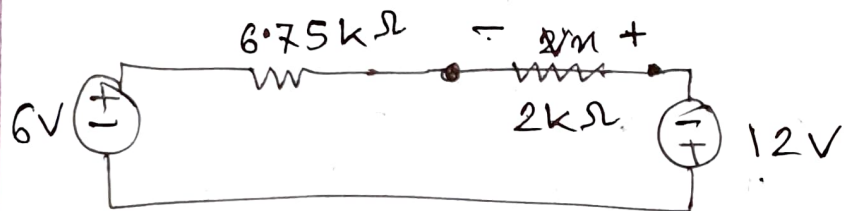$\hookrightarrow 0.75\text{ k}\Omega$  &  $6\text{ k}\Omega$




$\hookrightarrow 6\text{V}$  &  $12\text{V}$



$\therefore V_1 = 18\text{V}$

$R_1 = 6.7$

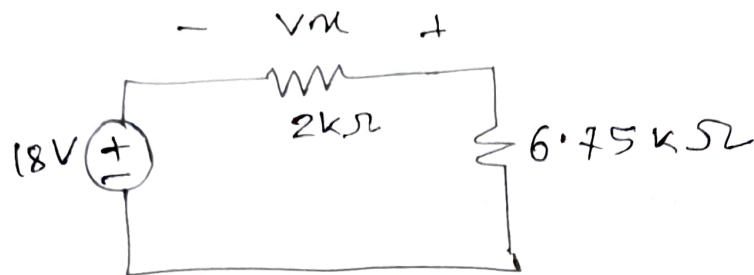

$$V_i = 18V$$

$$R_1 = 6.75k\Omega$$

$$\therefore V_x = \frac{2}{6.75 + 2} \times 18$$

$$= +4.114285$$


$$= -4.114285 \quad (\text{because of the } -V_x +)$$



### Problem 03:

For Thevenin we have to make open circuit then short circuit

Open circuit:

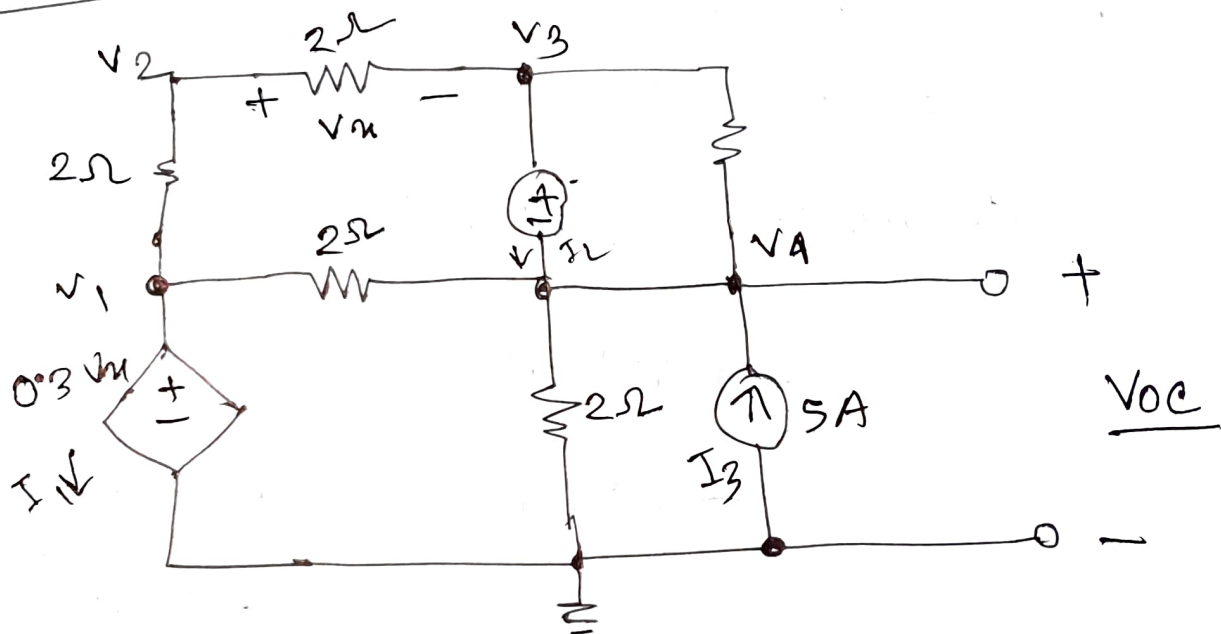

Equation for Node 01:

$$V_1 = 0.3 V_m$$

$$\Rightarrow V_1 - 0 = 0.3 V_m$$

$$\Rightarrow V_1 - 0.3 V_m = 0$$

$$\Rightarrow V_1 - 0.3 (V_2 - V_3) = 0$$

[From the circuit image]

For Node 02:

$$V_2 \left( \frac{1}{2} + \frac{1}{2} \right) - \frac{V_1}{2} - \frac{V_3}{2} = 0$$

Node 03:

$$V_3 \left( \frac{1}{2} + \frac{1}{2} \right) - \frac{V_2}{2} - \frac{V_4}{2} + I_2 = 0$$

Node 4:

$$V_4 \left( \frac{1}{2} + \frac{1}{2} + \frac{1}{2} \right) - \frac{V_1}{2} - \frac{V_3}{2} - \frac{0}{2} - I_3 - I_2 = 0 \quad \nearrow 5A$$

$$\Rightarrow V_4 \left( \frac{1}{2} + \frac{1}{2} + \frac{1}{2} \right) - \frac{V_1}{2} - \frac{V_3}{2} - 5 - I_2 = 0$$

~~Eq~~ Supernode  $V_3, V_4$

(could just ignore that I here)

$$V_4 \left( \frac{1}{2} + \frac{1}{2} + \frac{1}{2} \right) - \frac{V_1}{2} - \frac{V_3}{2} - 5 - I_2 + V_3 \left( \frac{1}{2} + \frac{1}{2} \right) - \frac{V_2}{2} - \frac{V_4}{2} + I_2 = 0$$

Equation for 4V source

$$V_3 - V_4 = 4V$$



Solving,  $V_1, V_2, V_{34}$  Supernod,  $V_3 - V_4$  with Calculator

$$V_1 = -1.14894$$

$$V_2 = 2.68085$$


$$V_3 = 6.51064$$

$$V_4 = 2.51064$$

We know, our  $V_{oc}$  is  $V_4$  here and the  $V_o$  ground

$$\therefore V_4 = V_{oc} = V_{th} = 2.51064$$

Now for short circuit

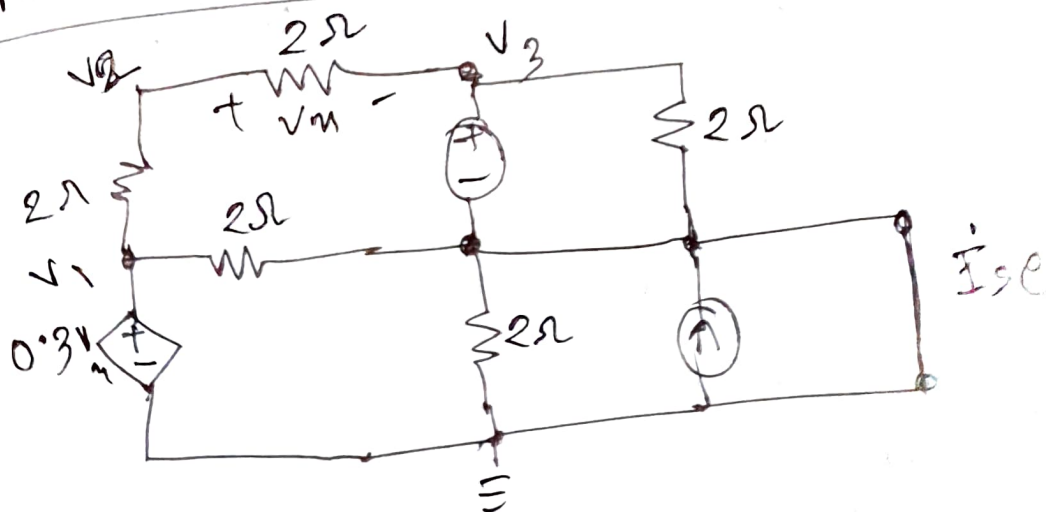

Here whole  ~~$v_4$~~   $v_4 = v_0$

$\therefore$  Node 01

$$v_1 - 0.3(v_2 - v_3) = 0 \quad (\text{from before})$$

Node 02:

$$v_2 \left( \frac{1}{2} + \frac{1}{2} \right) - \frac{v_1}{2} - \frac{v_3}{2} = 0$$

Node 03:

$$v_3 - v_4/v_0 = 4$$

$$\Rightarrow v_3 - 0 = 4$$

$$\Rightarrow v_3 = 4$$

Solving with calculator

$$v_1 = -0.705882$$

$$v_2 = 1.64706$$

$$v_3 = 4.0$$

$$\therefore I_1 = \frac{0 - (-0.705882)}{2} = 0.352941$$

$$I_2 = 5A$$

$$I_3 = \frac{-4}{2} = -2$$

$$\therefore I_{sc} = I_1 + I_2 + I_3$$

$$= 0.352941 + 5 - 2$$

$$= 3.352941$$

$$\therefore R_{th} = \frac{V_{th}}{I_{sc}}$$

$$[V_{th} = 2.51064]$$

$$= \frac{2.51064}{3.352941}$$

$$= 0.748787$$